

Traffic Light Controller



Prepared by

Ali Abdel Aleem Ali


Overview:

This project presents the design and implementation of a Traffic Light Controller based on a Finite State Machine (FSM) model. The controller is developed to manage traffic flow at a typical intersection by providing systematic switching between red, yellow, and green lights. Using FSM ensures a structured representation of states, transitions, and timing sequences, enabling efficient and predictable operation. The design is modeled in Verilog HDL and thoroughly verified through a testbench, which simulates different traffic scenarios to validate timing accuracy, correctness of state transitions, and overall system reliability. This FSM-based approach demonstrates how digital design techniques can be effectively applied to real-world traffic management systems, ensuring safety, robustness, and scalability for more complex intersections.

Design Procedure:


Design a traffic light controller for the intersection of Street A and Street B.

The controller uses a single synchronous clock domain. A clock divider produces a low-frequency tick, that enables the FSM to advance only once per tick, so green/yellow/red duration's map directly to real seconds. A synchronous, active-high reset initializes the system, and any asynchronous inputs are passed through a two-flip-flop synchronizer. This scheme improves timing predictability, simplifies simulation/testbench checks, and avoids metastability issues.

 

Each street has traffic sensors, which detect the presence of vehicles approaching or stopped at the intersection.

 The controller has 6 outputs (Ga, Ya, and Ra) drive the green, yellow and red lights on street A, and (Gb, Yb, and Rb) drive the corresponding lights on street B.




specification:

- If $S_a = 1$ means a vehicle approaching on street A.
- $S_b = 1$ means a vehicle is approaching on street B.
- Street A is a main street and has a green light until a car approaches on B, then the lights change, and B has a green light.
- At the end of 50 seconds, the lights change back unless there is a car on street B and none on A, in which case the B cycle is extended for 10 additional seconds.
- If cars continue to arrive on street B and no car appears on street A, B continues to have a green light.
- When A is green, it remains green at least 60 seconds, and then the lights change only when a car approaches on B.

FSM State Diagram:

Traffic Light FSM

 

Inputs and Outputs ports:

```
21
22
23 module traffic_light_controller(
24     input clk, reset_n,
25     input Sa, Sb,
26     output reg Ra, Ya, Ga,
27     output reg Rb, Yb, Gb
28 );
29
30
31 reg [3:0] state_reg, state_next;
32 localparam s0 = 0, s1 = 1, s2 = 2, s3 = 3,
33             s4 = 4, s5 = 5, s6 = 6, s7 = 7,
34             s8 = 8, s9 = 9, s10 = 10, s11 = 11,
35             s12 = 12;
36
```

Sequential State:

```
36
37 // Sequential state register
38 always @(posedge clk, negedge reset_n)
39 begin
40     if (~reset_n)
41         state_reg <= s0;
42     else
43         state_reg <= state_next;
44 end
45
```

Next State:

```
46 // Next state logic
47 always @(*)
48 begin
49     state_next = state_reg;
50     case(state_reg)
51         s0, s1, s2, s3, s4, s6, s7, s8, s9, s10:
52             state_next = state_reg + 1;
53         s5: if (~Sb)
54             state_next = s5;
55             else
56                 state_next = s6;
57         s11: if (~Sa & Sb)
58             state_next = s11;
59             else if(Sa | ~Sb)
60                 state_next = s12;
61         s12: state_next = s0;
62         default: state_next = s0;
63     endcase
64 end
65
```


Output Logic:


```

66 // Output logic
67 always @(*)
68 begin
69     Ra = 1'b0;
70     Ya = 1'b0;
71     Ga = 1'b0;
72     Rb = 1'b0;
73     Yb = 1'b0;
74     Gb = 1'b0;
75     case(state_reg)
76     s0, s1, s2, s3, s4, s5:
77         begin
78             Ga = 1'b1;
79             Rb = 1'b1;
80         end
81     s6:
82         begin
83             Ya = 1'b1;
84             Rb = 1'b1;
85         end
86     s7, s8, s9, s10, s11:
87         begin
88             Ra = 1'b1;
89             Gb = 1'b1;
90         end
91     s12:
92         begin
93             Ra = 1'b1;
94             Yb = 1'b1;
95         end
96     endcase
97 end
98 endmodule

```

RTL analysis:

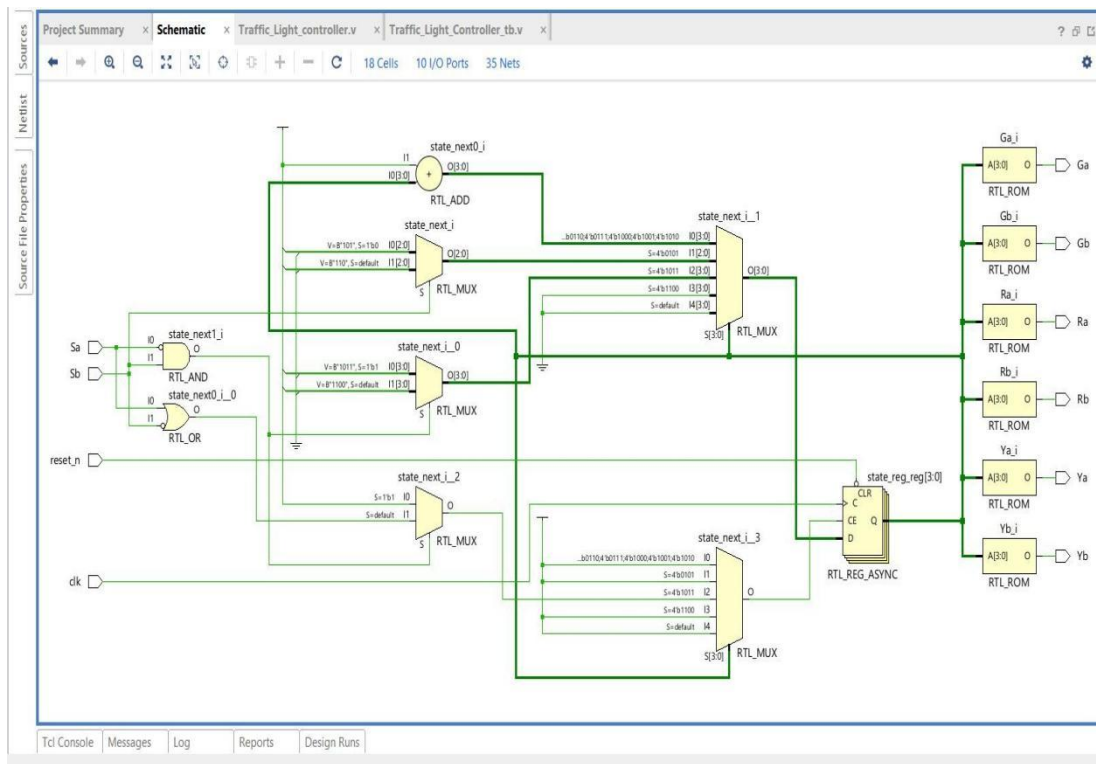

Testbench parameter:

```
23 module traffic_light_controller_tb(
24
25     );
26
27     reg clk, reset_n, Sa, Sb;
28     wire Ra, Ya, Ga;
29     wire Rb, Yb, Gb;
30
31
32     // Instantiate unit under test
33     traffic_light_controller CTRL0(
34         .clk(clk),
35         .reset_n(reset_n),
36         .Sa(Sa),
37         .Sb(Sb),
38         .Ra(Ra),
39         .Ya(Ya),
40         .Ga(Ga),
41         .Rb(Rb),
42         .Yb(Yb),
43         .Gb(Gb)
44     );
45
```

Assign new values to simpler the outputs:

```
46 // To make the output of the simulator simpler to read
47 // reduce the 6 different lights into light_A and light_B
48 // with values R, Y, G
49 wire [1:0] light_A, light_B;
50
51 localparam R = 0;
52 localparam Y = 1;
53 localparam G = 2;
54
55 assign light_A = Ra? R: Ya? Y: Ga? G: light_A;
56 assign light_B = Rb? R: Yb? Y: Gb? G: light_B;
57
58
```

Generate Clock:

```

58
59     // Generate stimuli
60
61     // Generating a clk signal
62     localparam T = 10;
63     S
64     begin
65         clk = 1'b0;
66         #(T / 2);
67         clk = 1'b1;
68         #(T / 2);
69     end

```

Reset condition and no cars in both street A, B:

```

68         #(T / 2);
69     end
70
71     initial
72     begin
73         // issue a quick reset for 2 ns
74         reset_n = 1'b0;
75         #2
76         reset_n = 1'b1;
77
78         // No cars at either streets
79         Sa = 0;
80         Sb = 0;
81

```

No cars at A, there is a car in B:

```

80      Sb = 0;
81
82      #80;
83
84      // No cars at A, Some cars at B
85      Sa = 0;
86      Sb = 1;
87      #100

```

Cars at both streets:

```

88
89      // Cars at both streets
90      Sa = 1;
91      Sb = 1;
92      #300;

```

Car appears at B, then no cars at either streets:


```

92      #300;
93
94      // Car appears at B, then no cars at either streets
95      Sa = 0;
96      Sb = 1;
97      #20;
98      Sb = 0;
99      Sa = 0;
100
101      #300 $stop;
102      end
103
104      endmodule
105

```


Simulation:

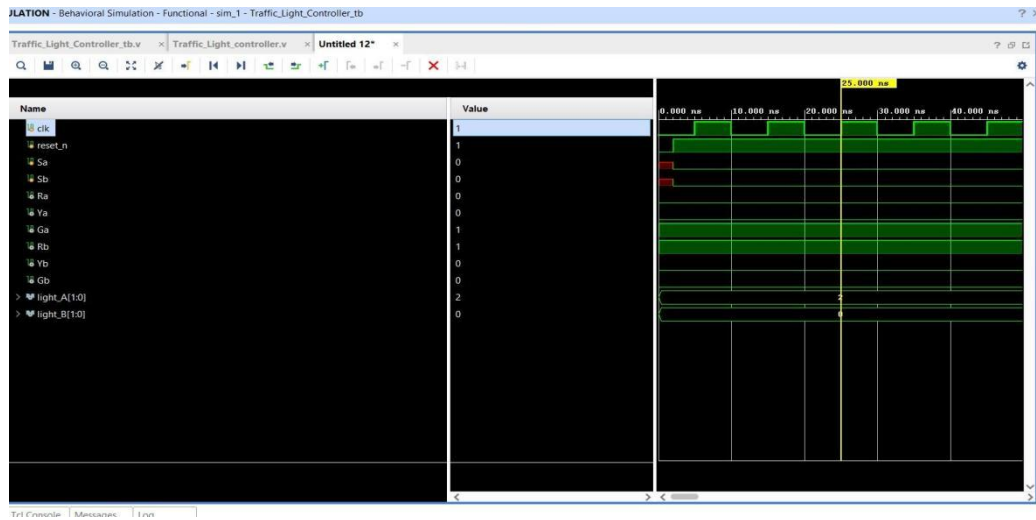- At the beginning no cars on both streets but A is main Street.




So: $GA\checkmark$ and $RB\checkmark$

- After, cars approach B:

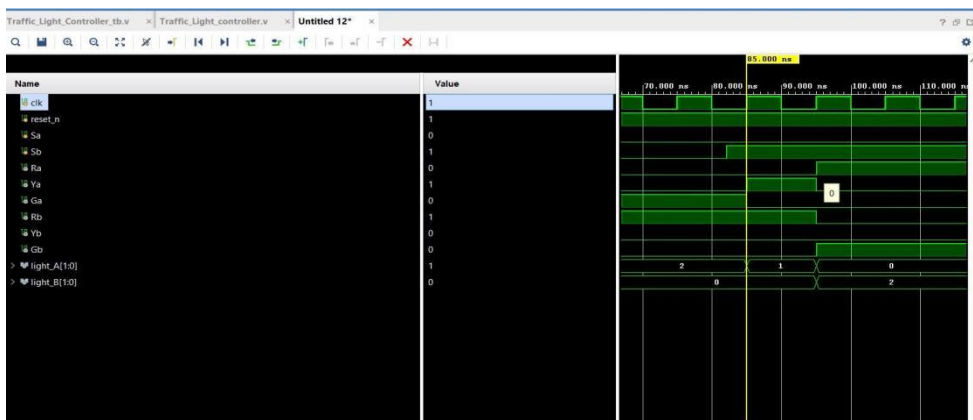

So, YA✓ and RB✓

- No cars at A, car approach B:

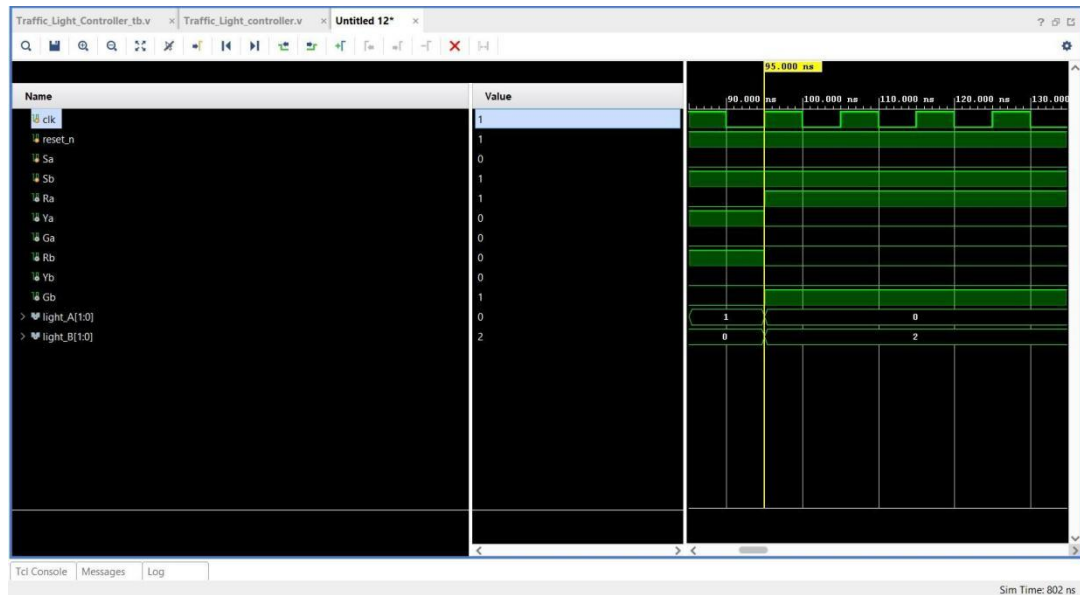

So, RA✓ and GB✓